

## Špecifikácia konfigurácie (Configuration Specifications)

*Špecifikácia konfigurácie* umožňuje špecifikovať výber deklarácie entity a tela architektúry pre danú inštanciu komponentu.

Všeobecný opis syntaxe *špecifikácie konfigurácie* má tvar:

```
configuration_specification ::=
    for instantiation_list : component_name binding_indication;

instantiation_list ::=  instantiation_label {, instantiation_label}
                       | others | all

binding_indication ::=
    [use entity_aspect]
    [generic map (generic_association-list)]
    [port map (port_association-list)]
entity_aspect ::=
    entity entity_name [(architecture_identifier)]
    | configuration configuration_name | open
```

**entity JKFF is**

```
    port(CLK, PRESET, CLEAR, J, K: Bit; Q, Q_bar: out Bit);
```

**end JKFF;**

**package Global\_signals is**

```
    signal CLK: Bit;
```

```
    signal PRESET: Bit;
```

```
    signal CLEAR: Bit;
```

**end Global\_signals;**

**entity Design is**

**end Design;**

**use Work.Global\_signals;**

**architecture Design of Design is**

```
    signal S1, S2, S3, S4: Bit;
```

```
    component FF
```

```
        port (J, K: Bit; Q, Q_bar: out Bit);
```

```
    end component;
```

```

for U0: FF use entity Work.JKFF
    port map(CLK => Global_signals.CLK,
              PRESET => Global_signals.PRESET,
              CLEAR => Global_signals.CLEAR,
              J=>J, K=>K, Q=>Q, Q_bar=>Q_bar);
begin
    U0: FF port map (S1, S2, S3, S4);
end Design;

```

```

entity Inverter is
    port (I1: in Bit; O1: out Bit);
end Inverter;
entity Inverter_user is
end Inverter_user;
architecture Inverter_user of Inverter_user is
    signal S: Bit;
    signal S_bar: Bit;
    component Inv
        port(In1: in Bit; Out1: out Bit);
    end component;
    for U1: Inv use entity Work.Inverter(Inverter_body)
        port map (I1 => In1, O1 => Out1);
begin
    U1: Inv port map (S, S_bar);
end Inverter_user;
architecture Inverter_body of Inverter is
begin
    O1 <= not I1 after 5 ns;
end Inverter_body;

```

## ***Deklarácia konfigurácie (Configuration Declaration)***

**configuration** Parts of Inverter\_user is

**for** Inverter\_user

**for** U1: Inv

**use entity** Work.Inverter(Inverter\_body)

**port map** (I1 => In1, O1 => Out1);

**end for;**

**end for;**

**end** Parts;

**configuration** FULL\_SLOT of COMM\_BOARD is

**attribute** KIND of COMM\_BOARD: **entity is** FULL\_SIZE;

**for** LOW\_COST -- an architecture of COMM\_BOARD

**for** CPU: PROCESSOR

**use entity** STD\_PARTS.SPARC (Fujitsu)

**generic map** (Clock => 40ns);

**end for;** -- for PROCESSOR

**for** BUS\_CONTROLLER

**for** Protocol\_Chip: IEEE\_488

**use entity** STD\_PARTS.NEC;

**end for;**

**end for;** -- for BUS\_CONTROLLER

...

**end for;** -- for LOW\_COST

**end** FULL\_SLOT;

**for** CPU: PROCESSOR **use entity** STD\_PARTS.SPARC (Fujitsu)

**generic map** (Clock => 40ns);

**for** Fujitsu

-- component configurations for instantiations,

-- or block configurations for blocks in Fujitsu

**end for;**

**end for;** -- for PROCESSOR

**for** B1: BUS\_CONTROLLER

**use entity** COMPANY\_LIBRARY.STD\_CONTROLLER (Std\_body);

**for** Std\_body

**for** Protocol\_Chip: IEEE\_488

**use entity** STD\_PARTS.NEC;

**end for**;

**end for**;


**end for**;

**for** B:COMM\_BOARD

**use configuration** HALF\_SLOT;

**end for**;

# KNIŽNICE

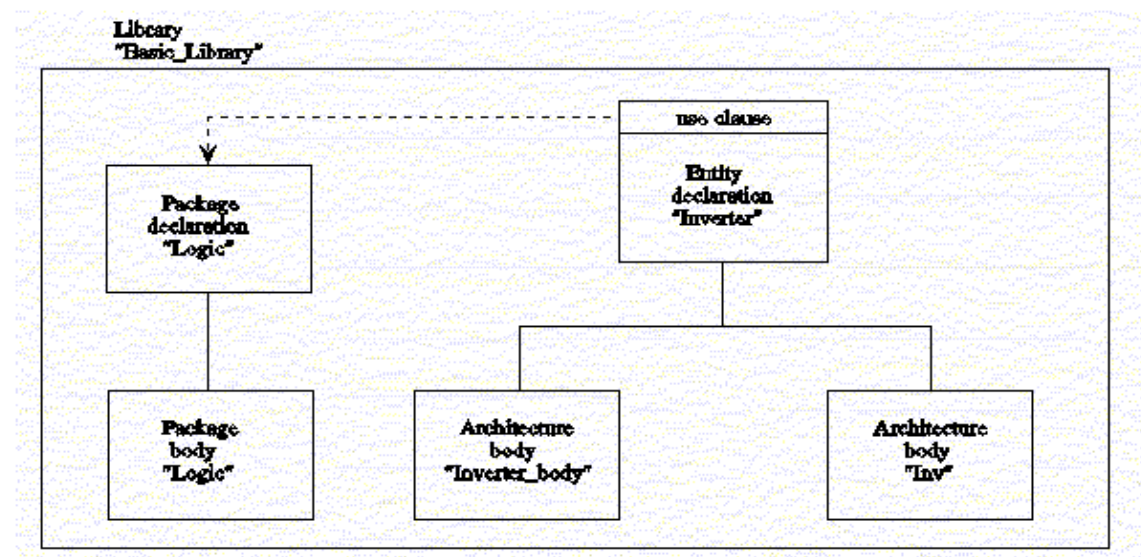


```
use Basic_library.Logic;
```

```
use Logic.all;
```

```
entity Inv is
```

```
port(X:in Three_level_logic;Y:out Three_level_logic);
```

```
end Inv;
```

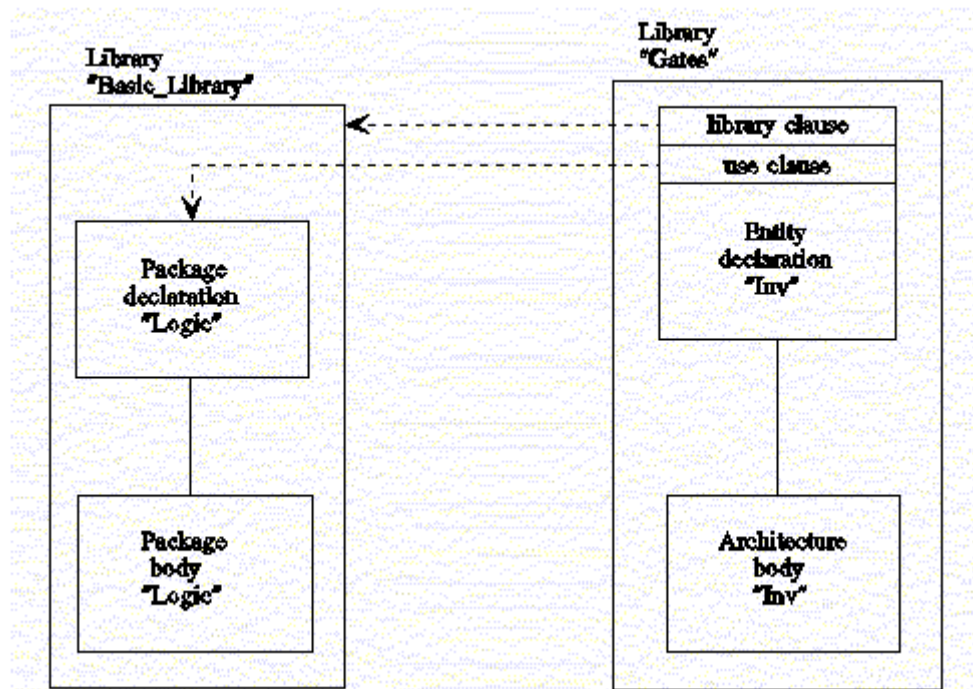

```

library Basic_library;
use Basic_library.Logic;
use Logic.all;
entity Inverter is
port(X:in Three_level_logic;Y:out Three_level_logic);
end Inverter;

```

Konštrukcie, ktoré vytvárajú nový *deklaračný región*:

- Deklarácia entity a k nej priradená architektúra.
- Príkaz blok.
- Príkaz proces.
- Balík.
- Podprogram.
- Konfigurácia.
- Typy záznam.
- Príkaz cyklu.
- Deklarácia komponentu.

-- a block declaration

B1: **block**

-- containing a signal declaration

**signal** SUM, I1, I2: Bit;

**begin**

-- a nested block declaration

**B2: block**

-- This SUM hides the one in block B1,

**signal** SUM: Bit;

**begin**

-- so this assigns to the SUM in B2,

SUM <= I1 **and** I2 **after** 5.5 ns;

-- whereas this would assign to the SUM in B1.

-- B1.SUM <= I1 **and** I2 **after** 5.5 ns;

**end block;**

-- And this assigns to the SUM in B1.

SUM <= I1 **and** I2 **after** 5.5 ns;

**end block;**

Ilustračný príklad:

**package SIG is**

**signal** X: INTEGER:= 1;

**end;**

**use** WORK.SIG;

**entity Y is**

**signal** X: INTEGER:= 2;

**end Y;**

**architecture Z of Y is**

**signal** Z1, Z2, Z3, Z4, Z5: INTEGER:= 0;

**function** R **return** INTEGER **is**

**variable** X: INTEGER:= 3;

**begin**

**return** X;

**end R;**

**begin**

**B: block**

**signal** X: INTEGER:= 4;

**signal** Z6: INTEGER:= 0;

**begin**

        Z6 <= X + Y.X;

**end block B;**

**process**

**variable** X: INTEGER:= 5;

**begin**

        Z5 <= X;

**wait;**

**end process;**

    Z1 <= WORK.SIG.X;

    Z2 <= X;


    Z3 <= R;

    Z4 <= B.X;



**end Z;**

### Náhradné hodnoty (Default Values)

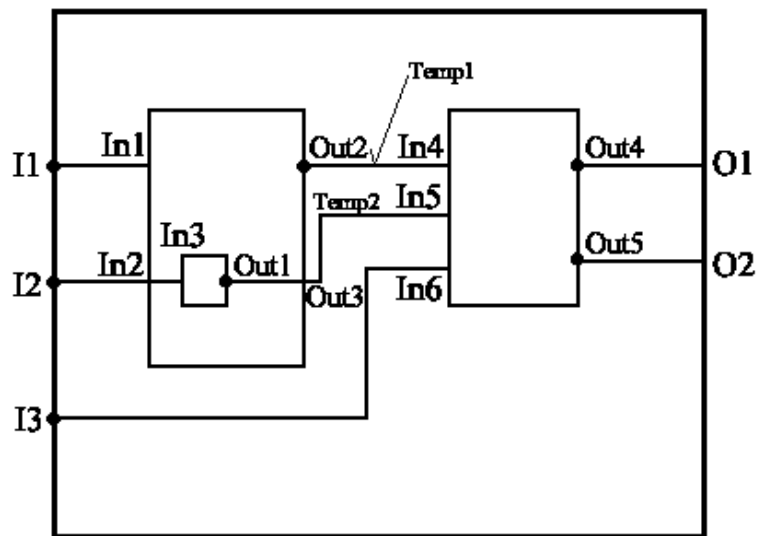

```
package Three_level_logic is  
    type Three is ('X', '0', '1');  
    function Inv (Q: Three) return Three;  
end Three_level_logic;  
package body Three_level_logic is  
    function Inv (Q: Three) return Three is  
    begin  
        case Q is  
            when 'X' =>  
                return 'X';  
            when '0' =>  
                return '1';  
            when '1' =>  
                return '0';  
        end case;  
    end Inv;  
end Three_level_logic;  
use Work.Three_level_logic.all;  
entity Inverter is  
    port (P1: Three := 'X'; P2: out Three := 'X');
```

```

end Inverter;
use Work.Three_level_logic.all;
entity Buf is
    port (P1: Three := 'X'; P2: out Three := 'X');
end Buf;
architecture Inverter of Inverter is
begin
    P2 <= Inv (P1) after 5 ns;
end Inverter;
architecture Buf of Buf is
begin
    P2 <= P1 after 5 ns;
end Buf;
use Work.Three_level_logic.all;
entity Oscilator is
end Oscilator;
architecture Oscilator of Oscilator is
    component Inverter
        port (P1: Three; P2: out Three);
    end component;
    component Buf
        port (P1: Three; P2: out Three);
    end component;
    for all : Inverter use entity Work.Inverter(Inverter);
    for all : Buf use entity Work.Buf(Buf);
    signal S1 : Three := '0';
    signal S2 : Three := '1';
begin
    U1 : Inverter port map (S1, S2);
    U2 : Buf port map (S2, S1);
end Oscilator;

```

## Nekompatibilita typov

```
function Bit4_to_BIT (b: in Bit4) return BIT
is begin
    case b is
        when '0' => return '0';
        when '1' => return '1';
        when 'X' => return '0';
        when 'Z' => return '0';
    end case;
end Bit4_to_BIT;
```

```
function BIT_to_Bit4 (b: in BIT) return Bit4
is begin
    case b is
        when '0' => return '0';
        when '1' => return '1';
    end case;
end BIT_to_Bit4;
```

**signal** C: Bit;

**port** (CLEAR: Bit4.....);

**port map** (CLEAR => BIT\_to\_Bit4( C) .....);

**signal** FF\_OUT: Bit;

**port** (Q: inout Bit4.....);

**port map** (Bit4\_to\_BIT( Q) => BIT\_to\_Bit4( FF\_OUT).....);

## Návrh kombinačnej logiky a automatická syntéza

### Multiplexor

entity MUX4TO1 is

```
port( A,B,C,D,S0,S1 : in BIT;
```

```
      Y : out BIT);
```

```
end MUX4TO1;
```


-- Concurrent signal assignment

architecture DATAFLOW1 of MUX4TO1 is

begin

-- parentheses required when mixing operators of equal precedence
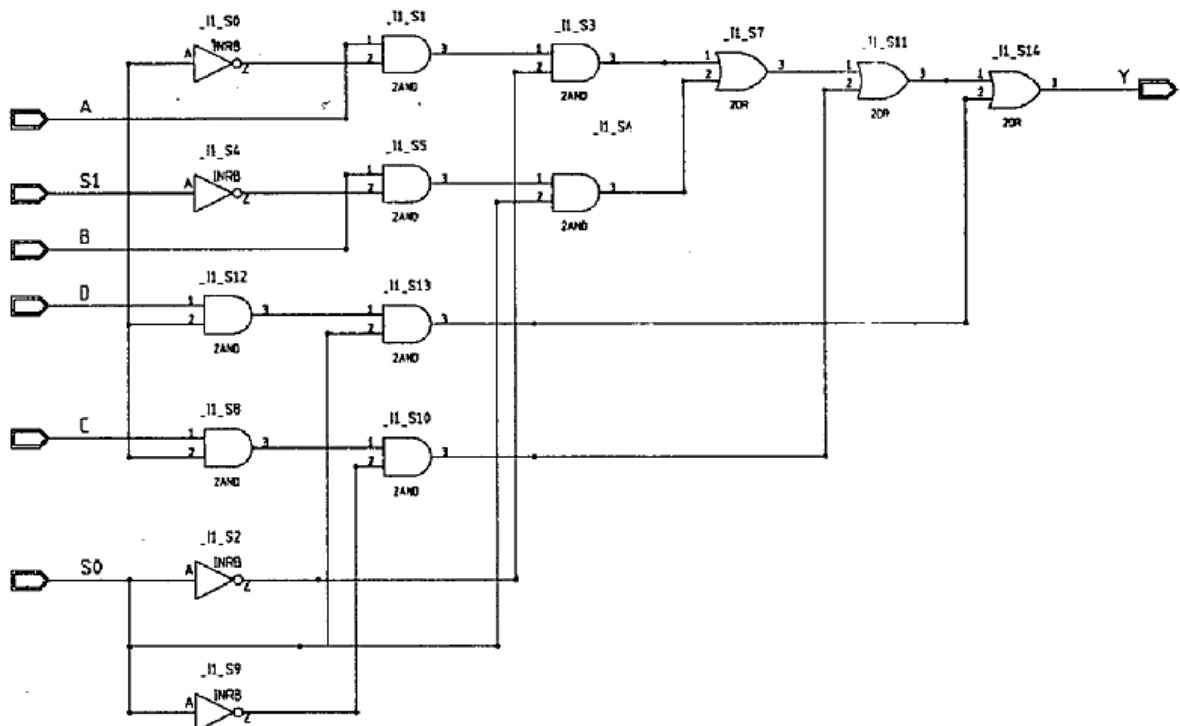
```
Y<=(A and not S1 and not S0) or (B and not S1 and S0) or  
(C and S1 and not S0) or (D and S1 and S0);
```



DATAFLOW1 synthesized circuit.


```
end DATAFLOW1;
```

-- Concurrent signal assignment with additional parentheses  
architecture DATAFLOW2 of MUX4TO1 is

begin

-- extra parentheses control the order of evaluation/structure of the circuit

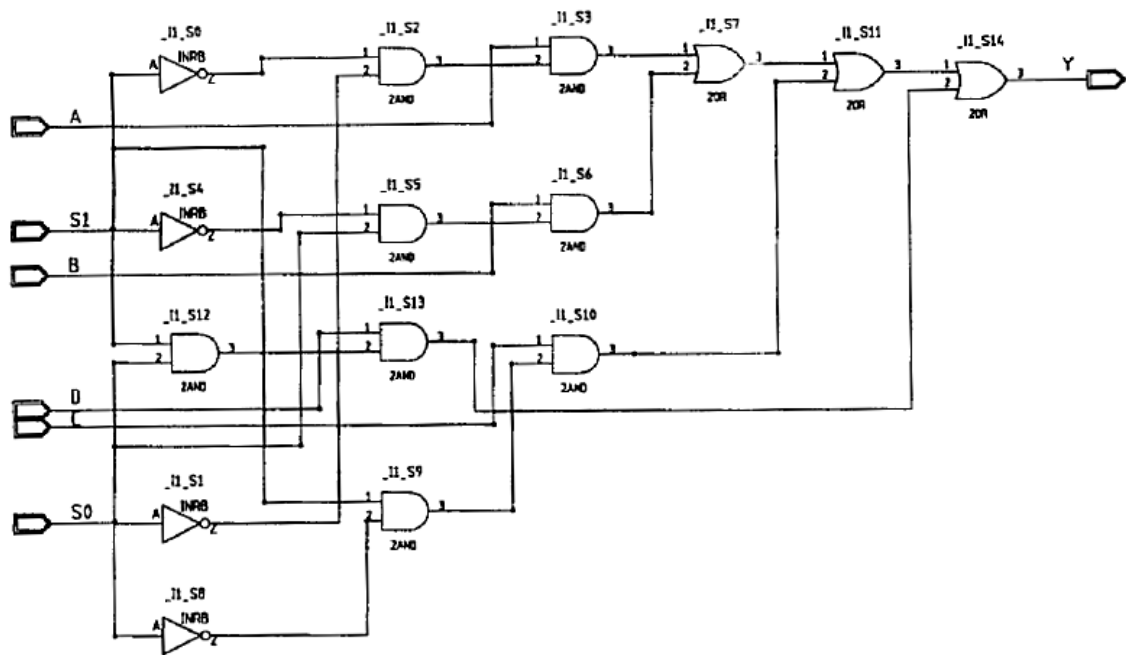Y<= (A and (not S1 and not S0)) or (B and (not S1 and S0)) or  
(C and (S1 and not S0)) or (D and (S1 and S0));



DATAFLOW2 synthesized circuit.

end DATAFLOW2;

-- Conditional signal assignment  
architecture DATAFLOW3 of MUX4TO1 is

begin

-- each branch condition may be different

Y<= A when (S1='0' and S0='0') else

B when (S1='0' and S0='1') else

C when (S1='1' and S0='0') else

D;

end DATAFLOW3;



-- Selected signal assignment

architecture DATAFLOW4 of MUX4TO1 is

signal SEL : BIT\_VECTOR(1 downto 0);

begin

-- each branch tests for a different value of the same condition  
with SEL select

Y <= A when 00,


B when 01,

C when 10,


D when 11;

SEL <= S1&S0;


end DATAFLOW4;

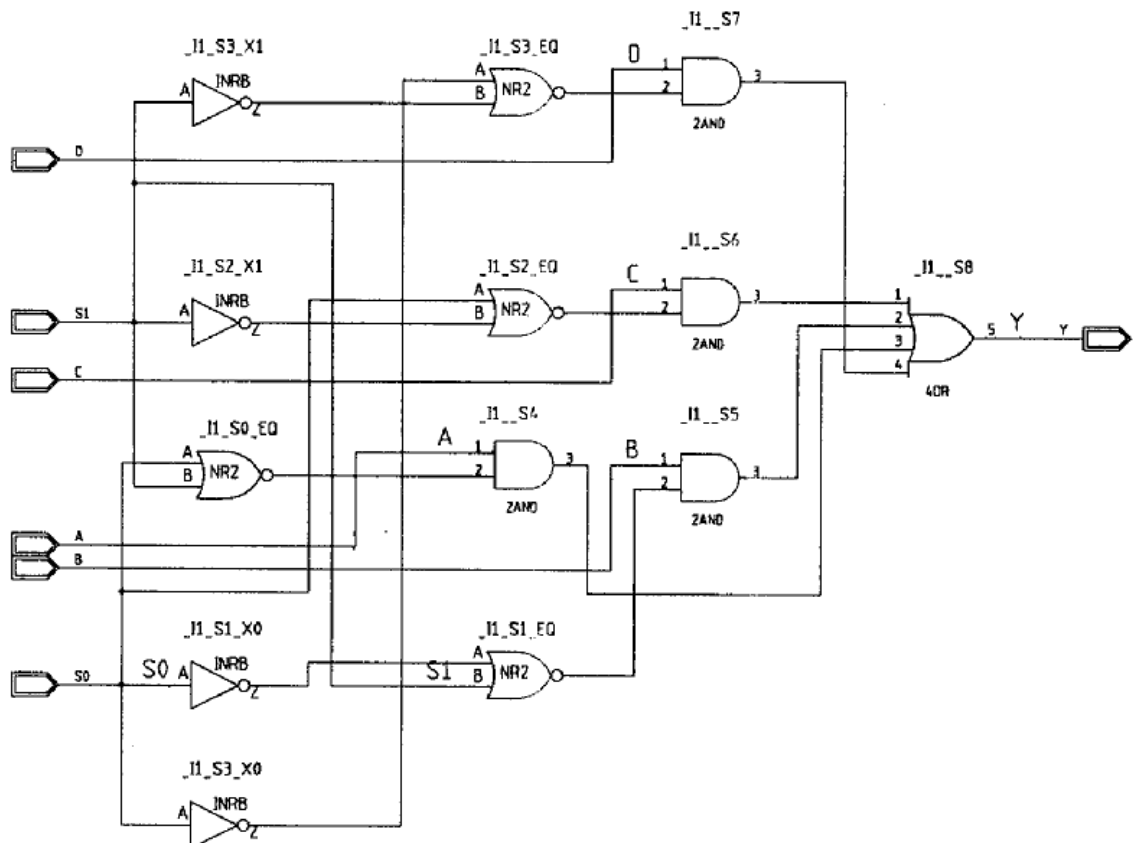

DATAFLOW4 synthesized circuit.

 

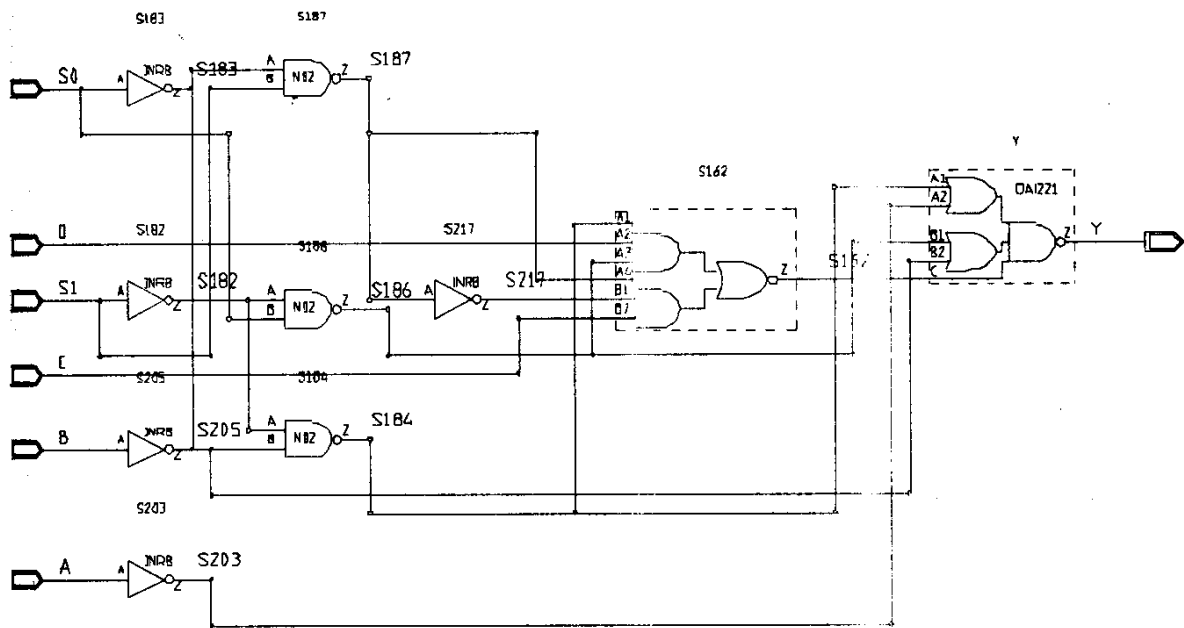**DATAFLOW1, DATAFLOW2 and DATAFLOW4 optimized circuit.**



**DATAFLOW3 optimized circuit.**



**Table 4.4** Logic synthesis and optimization statistics for the dataflow style architecture

<i>Parameters</i>	<i>Synthesis</i>	<i>Optimization</i>
<i>Temperature: 25.0 °C</i>	<i>Library: generic</i>	<i>Type: area</i>
<i>Voltage: 5.0V</i>		<i>Level: low</i>
<b>Circuit: MUX4TOI-DATAFLOW1</b>		
<b>Cells</b>	<b>15</b>	<b>5</b>
<b>Transistors</b>	<b>74</b>	<b>28</b>
<b>Area</b>	<b>9154.08</b>	<b>3344.76</b>
<b>Longest input to output delay</b>	<b>(S1 to Y) 3.171 ns</b>	<b>1.568 ns</b>
<b>Circuit : MUX4TOI-DATAFLOW2</b>		
<b>Cells</b>	<b>15</b>	<b>5</b>
<b>Transistors</b>	<b>74</b>	<b>28</b>
<b>Area</b>	<b>9154.08</b>	<b>3344.76</b>
<b>Longest input to output delay</b>	<b>(S0 to Y) 3.171 ns</b>	<b>1.568 ns</b>
<b>Circuit: MUX4TOI-DATAFLOW3</b>		
<b>Cells</b>	<b>19</b>	<b>10</b>
<b>Transistors</b>	<b>90</b>	<b>44</b>
<b>Area</b>	<b>11266.56</b>	<b>5809.32</b>
<b>Longest input to output delay</b>	<b>(S0 to Y) 4.619 ns</b>	<b>2.967 ns</b>
<b>Circuit: MUX4TOI-DATAFLOW4</b>		
<b>Cells</b>	<b>13</b>	<b>5</b>
<b>Transistors</b>	<b>58</b>	<b>28</b>
<b>Area</b>	<b>7393.68</b>	<b>3344.76</b>
<b>Longest input to output delay</b>	<b>(S1 to Y) 2.292</b>	<b>1.568</b>

entity MUX4TO1 is

port (A, B, C, D : in BIT;

S : in BIT\_VECTOR(1 downto 0); -- array type inputs

Y : out BIT );

end MUX4TO1;

architecture CASE1 of MUX4TO1 is

begin

process (A,B,C,D,S(1 downto 0))

begin

case S is

when "00" => Y <= A;

when "01" => Y <= B;


when "10" => Y <= C;

when "11" => Y <= D;


end case;

end process;


end CASE1;

 

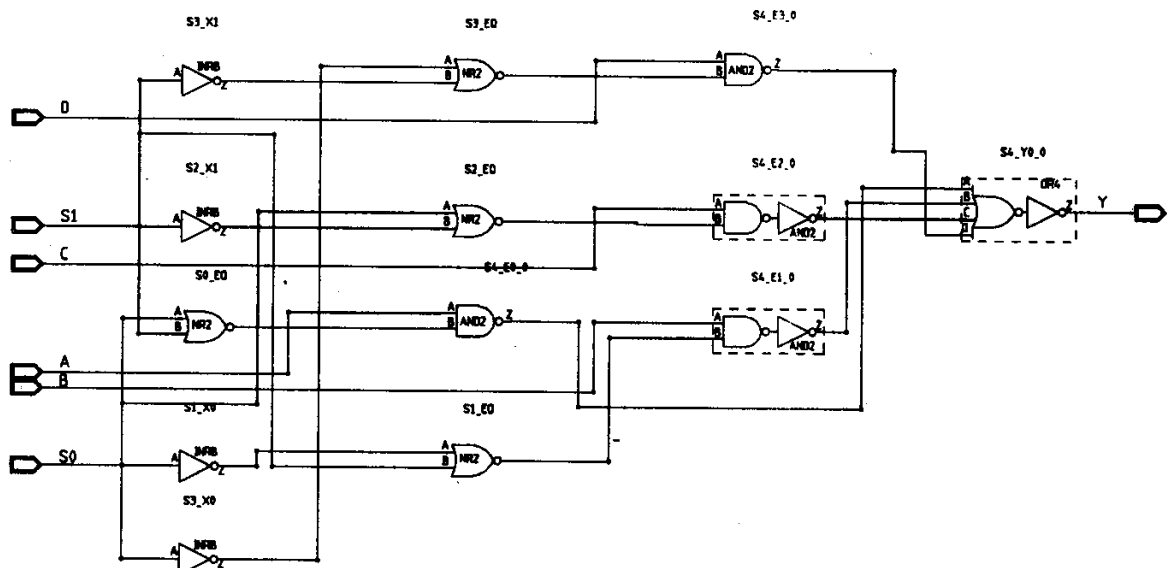Top-level circuit for CASE and IF\_ELSE architectures.



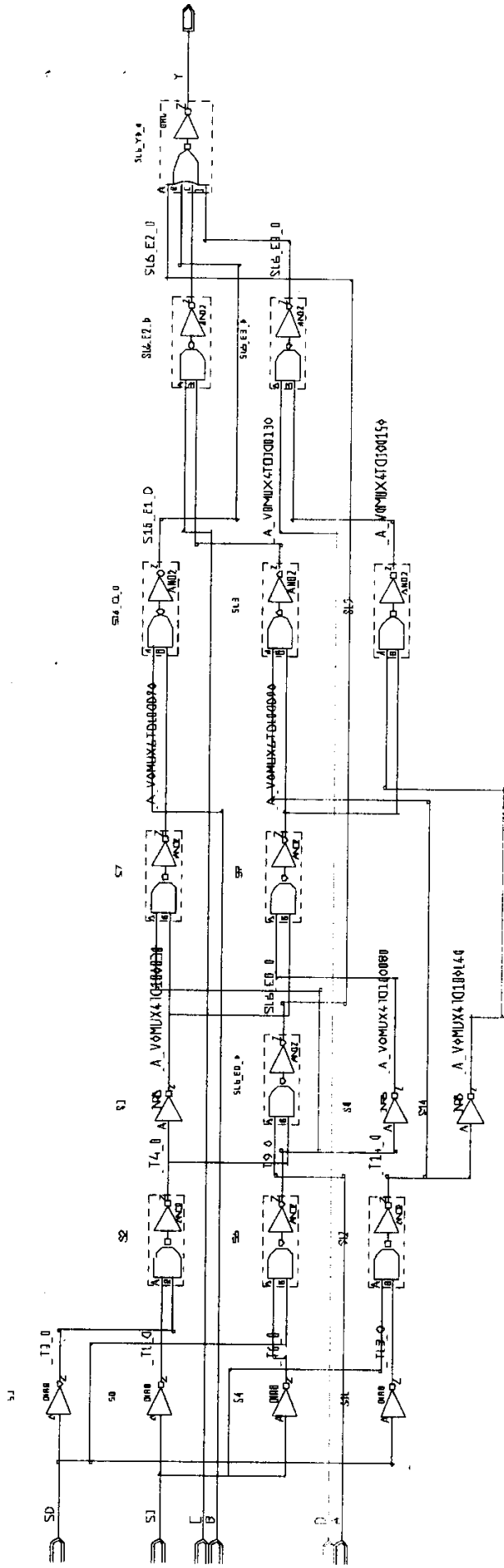Second level of the synthesized CASE1 circuit.



Second level of the synthesized IF\_ELSE circuit.

**architecture IF\_ELSE of MUX4TO1 is**

**begin**

**process (A,B,C,D,S(1 downto 0))**

**begin**

**if (S(1)='0' and S(0)='0') then**

**Y <= A;**

**elsif (S(1)='0' and S(0)='1') then**

**Y <= B;**

**elsif (S="10") then**

**Y <= C;**

**else**

**Y <= D;**

**end if;**

**end process;**

**end IF\_ELSE;**

**-- The Case statement using a variable in the process**

**architecture CASE2 of MUX4TO1 is**

**begin**

**process (A,B,C,D,S(1 downto 0))**

**variable TEMP : BIT;**

**begin**

**case S is**

**when "00" => TEMP := A;**

**when "01" => TEMP := B;**

**when "10" => TEMP := C;**

**when "11" => TEMP := D;**

**end case;**

**-- The variable is not visible outside of the process.**

**Y <= TEMP;**

**end process;**

**end CASE2;**


-- The Case statement using a local signal architecture CASE3 of MUX4TO1 is

```

signal TEMP : BIT;
begin
  process (A,B,C,D,S(1 downto 0))
    begin
      case S is
        when "00" => TEMP <= A;
        when "01" => TEMP <= B;
        when "10" => TEMP <= C;
        when "11" => TEMP <= D;
      end case;
    end process;
    Y <= TEMP;
  end CASE3;

```

 -- A concurrent signal assignment is used to pass the result out to Y.




Top level circuits for the CASE2 and CASE3 architectures.

**Table 4.5** Logic synthesis and optimization statistics for the behavioural style architecture

<i>Parameters</i>	<i>Synthesis</i>	<i>Optimization</i>
<i>Temperature: 25.0 °C</i>	<i>Library : generic</i>	<i>Type: area</i>
<i>Voltage: 5.0 V</i>		<i>Level: low</i>
<b>Circuit: MUX4TOI-CASE1</b>		
Cells	13	5
Transistors	58	28
Area	7393.68	3344.76
Longest input to output delay	(S0 to Y) 2.292	1.568 ns
<b>Circuit: MUX4TOI-IF_ELSE</b>		
Cells	19	10
Transistors	90	44
Area	11266.56	5809.32
Longest input to output delay	(S0 to Y) 4.619 NS	2.967 ns
<b>Circuit: MUX4TOI-CASE2</b>		
Cells	13	5
Transistors	58	28
Area	7393.68	3344.76
Longest input to output delay	(S0 to Y) 2.292 NS	1.561 ns
<b>Circuit: MUX4TOI-CASE3</b>		
Cells	13	5
Transistors	58	28
Area	7393.68	3344.76
Longest input to output delay	(S0 to Y) 2.292 NS	1.561 ns

## Návrh sekvenčnej logiky

### 4-bitový posuvný register

 

Simple 4-bit shift register.

```
--balík analyzovaný do knižnice USER_UTILS  
package NEW_TYPE_DEFS is  
  subtype HALF_REG is BIT_VECTOR(1 to 4);  
end NEW_TYPE_DEFS;
```

```
library USER_UTILS;  
use USER_UTILS.NEW_TYPE_DEFS.all;
```


```
entity FOUR_SHIFT is  
  port (X : in BIT;  
        CLK, INIT : in BIT;  
        Z : out BIT );  
end FOUR_SHIFT;
```

```
architecture STRING_ASSIGN of FOUR_SHIFT is  
  signal REG : HALF_REG;  
begin  
  process (X, CLK, INIT)  
  begin  
    if (not CLK'stable and CLK='1') then  
      if INIT='1' then  
        REG <= X & REG(1 to 3);  
      else  
        REG <= "1000";  
      end if;  
    end if;  
  end process;  
  Z <= not REG(4);  
end STRING_ASSIGN;
```


```

-- edge-triggered synchronous process
architecture SYNC_WAIT of FOUR_SHIFT is
signal REG : HALF_REG;
begin
  process
  begin
    wait until (CLK'event and CLK='1');
    if (INIT='1') then
      REG <= X & REG(1 to 3);
    else
      REG <= "1000";
    end if;
  end process;
  Z <= not REG(4);
end SYNC_WAIT;


```

 

 Top-level synthesized circuits for the architectures STRING\_ASSIGN, ASYNC\_IF1, ASYNC\_IF2 and SYNC\_WAIT.



 Synthesized circuit described by the process in both the STRING\_ASSIGN and SYNC\_WAIT architectures.




Optimized circuit for the STRING\_ASSIGN and SYNC\_WAIT architectures. Each two-level hierarchy has been flattened.




```

-- Independent asynchronous initialization
architecture ASYNC_IF1 of FOUR_SHIFT is
signal REG : HALF_REG;
begin
  process (X, CLK, INIT)
  begin
    if (INIT='0') then
      REG <= (1, others=>0);
    end if;
    if (CLK'event and CLK='1') then
      if (INIT='1') then
        REG <= X & REG(1 to 3);
      end if;
    end if;
  end process;
  Z <= not REG(4);
end ASYNC_IF1;

```

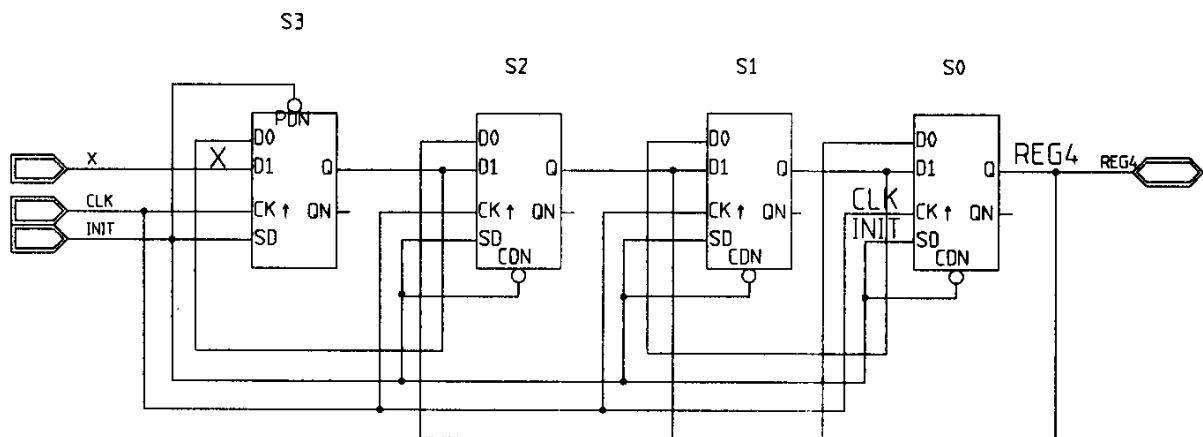

 Synthesized circuit described by the process in the ASYNC\_IF1 architecture.




Optimized circuit (with flattened hierarchy) for the ASYNC\_IF1 architecture.


```

-- Asynchronous initialization combined with the synchronous section
architecture ASYNC_IF2 of FOUR_SHIFT is
signal REG : HALF_REG;
begin
  process (X, CLK, INIT)
  begin
    if (INIT='0') then
      REG <= (1,0,0,0);
    elsif (CLK'event and CLK='1') then
      REG <= X & REG(1 to 3);
    end if;
  end process;
  Z <= not REG(4);
end ASYNC_IF2;

```

 

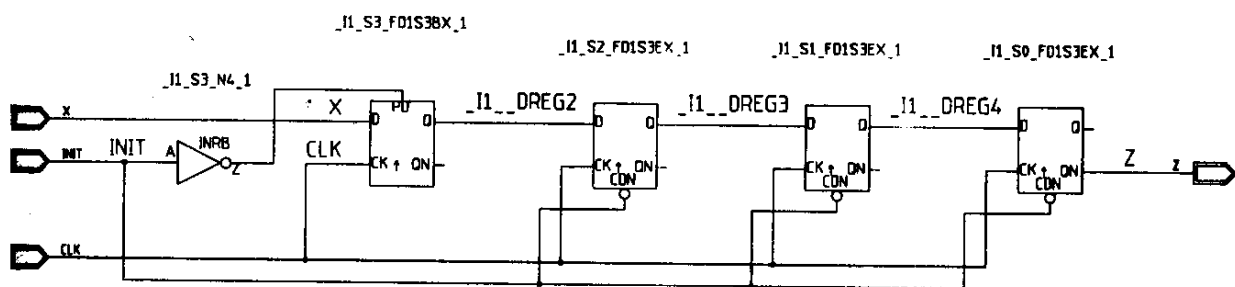Synthesized circuit described by the process in the ASYNC\_IF2 architecture.



Optimized circuit (with flattened hierarchy) for the ASYNC\_IF2 architecture.

**Table 5.1** Logic synthesis and optimization statistics for two synchronous and two asynchronous behavioural style architectures

<i>Parameters</i>	<i>Synthesis</i>	<i>Optimization</i>
Temperature: 25.0 °C	Library: generic	Type: area
Voltage: 5.0 V		Level: low
<b>Circuit: FOUR_SHIFT-STRING_ASSIGN FOUR_SHIFT-SYNC_WAIT</b>		
Cells	11	9
Transistors	106	98
Area	13379	12322
Longest latch to latch delay	2.297	No change
<b>Circuit: FOUR_SHIFT-ASYNC_IF1</b>		
Cells	5	10
Transistors	138	124
Area	15843	15491
Longest latch to latch delay	2.775	3.082
<b>Circuit: FOUR_SHIFT-ASYNC_IF2</b>		
Cells	5	No change
Transistors	92	90
Area	11794	11618
Longest latch to latch delay	1.813	No change

```

entity DFF is
  port (D : in BIT;
        CLK, PC : in BIT;
        Q, QBAR : out BIT);
end DFF;

```

-- D-type with synchronous clear, behavioral description

architecture BEHAVIOR of DFF is

```

signal INTERNAL_Q : BIT;

```

```

begin

```

```

  -- outputs assigned concurrently (outside) the process

```

```

  Q <= INTERNAL_Q;

```

```

  QBAR <= not INTERNAL_Q;

```

```

  process

```

```

  begin

```

```

    wait until (CLK'event and CLK='0');

```

```

    if (PC='0') then

```

```

      INTERNAL_Q <= '0'

```

```

    else

```

```

      INTERNAL_Q <= D;

```

```

    end if;

```

```


  end process;

```

```

end BEHAVIOR;

```

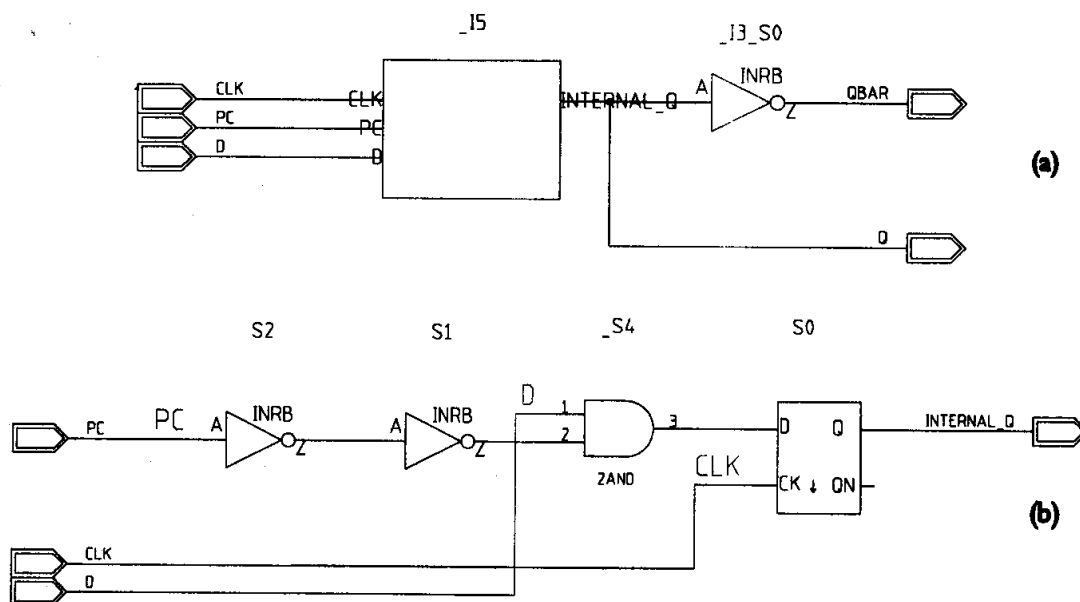

Synthesized DFF architectural description. (a) Top-level circuit. (b) Circuit described by the Process statement.

```

entity JKFF is
  port (J, K : in BIT;
        CLK, PC : in BIT;
        Q, QBAR : out BIT);
end JKFF;



```

architecture BEHAVIOR of JKFF is

```

signal S : BIT;
begin
  Q <= S;
  QBAR <= not S;
  process
    variable JK : BIT_VECTOR(0 to 1);
  begin
    wait until (CLK'event and CLK='0');
    JK := J & K;
    if (PC='0') then
      S <= '0';
    else
      case JK is
        when "00" => S <= S;
        when "10" => S <= '1';
        when "01" => S <= '0';
        when "11" => S <= not S;
      end case;
    end if;
  end process;
end BEHAVIOR;

```

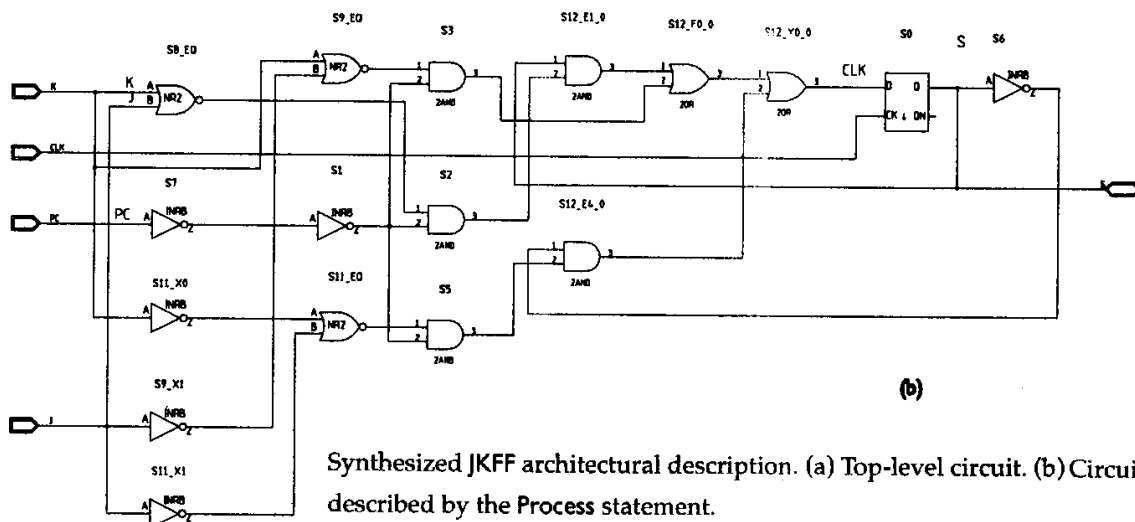 

Synthesized JKFF architectural description. (a) Top-level circuit. (b) Circuit described by the Process statement.

**Table 5.3** Logic synthesis and optimization statistics for the D- and JK-type user-defined components

<i>Parameters</i>	<i>Synthesis</i>	<i>Optimization</i>
<i>Temperature: 25.0 °C</i>	<i>Library: generic</i>	<i>Type: area</i>
<i>Voltage: 5.0 V</i>		<i>Level: low</i>
<b>Circuit: DFF-BEHAVIOUR</b>		
Cells	5	2
Transistors	30	24
Area	4048	2992
Longest input to latch delay	1.942	1.304
<b>Circuit: JKFF-BEHAVIOUR</b>		
Cells	18	4
Transistors	86	34
Area	11266	4224
Longest input to latch delay	4.214	2.294

**Table 5.4** Logic synthesis and optimization statistics for the structural style architectures. Manually instantiated D-type and regular /irregular generated JK-type structures. All components are the optimized versions

<i>Parameters</i>	<i>Synthesis</i>	<i>Optimization</i>
<i>Temperature: 25.0 °C</i>	<i>Library: generic</i>	<i>Type: area</i>
<i>Voltage: 5.0 V</i>		<i>Level: low</i>
<b>Circuit: FOUR_SHIFT-STRUCTURAL</b>		
Cells	8	No change
Transistors	96	No change
Area	11970	No change
Longest latch to latch delay	2.684	No change
<b>Circuit: FOUR_SHIFT-REG_GEN FOUR_SHIFT-IRREG_GEN</b>		
Cells	17	13
Transistors	138	122
Area	17251	15139
Longest latch to latch delay	4.353	4.240

architecture BAD1 of DFF is

begin

process

begin


wait until (CLK'event and CLK= '0');

Q <= D;

QBAR <= not D;

end process;

end BAD1;

 


Synthesized circuit produced by BAD1.

architecture BAD2 of DFF is

```

begin
  process
    begin
      wait until (CLK'event and CLK= '0');
      Q <= D;
    end process;
    QBAR <= not D;
  end BAD2;

```

 

Synthesized circuit produced by BAD2.

architecture BAD\_JK of JKFF is

```

signal S, SBAR : BIT;
begin
  process
    variable JK : BIT_VECTOR(0 to 1);
    begin
      wait until (CLK'event and CLK= '0');
      JK:= J&K;
      case JK is
        when "00" => S<= S;
        when "10" => S<= '1';
        when "01" => S<= '0';
        when "11" => S<= not S;
      end case;
      SBAR <= not S;
    end process;
    Q <= S;
    QBAR <= SBAR;
  end BAD_JK;

```